

3. The circuit on the right shows two identical resistors in parallel.

Calculate the power of resistor A.

To answer this question you will first need to work out the potential difference across resistor A.

